

# Differential Equations

## Lecture 9

Sahraei

Physics Department

<http://www.razi.ac.ir/sahraei>

## Review of lecture 8

# Linear Equations

$$\frac{dy}{dx} + p(x)y = Q(x) \quad *$$

$$y = e^{-\int p dx} \left( \int e^{\int p dx} Q(x) dx + c \right)$$

is the general solution of \*

As we have seen, the general second order differential equation has the form:

$$F(x, y, y', y'') = 0$$

## Solving 2<sup>nd</sup> Order Linear Equation

Try reducing to first order equations.  
This works for equations of the form:

Case 1-Dependent variable missing  $f(x, y', y'') = 0$

$$y' = p, \quad y'' = \frac{dp}{dx} \quad f\left(x, p, \frac{dp}{dx}\right) = 0$$

Case 2-Independent variable missing  $g(y, y', y'') = 0$

$$y' = p, \quad y'' = \frac{dp}{dx} = \frac{dp}{dy} \frac{dy}{dx} = p \frac{dp}{dy} \quad g\left(y, p, p \frac{dp}{dy}\right)$$

Problems page 57-1a

$$yy'' + (y')^2 = 0$$

$$f(y, y', y'') = 0$$

$$y' = \frac{dy}{dx} = p$$

$$y'' = \frac{dp}{dx} = \frac{dp}{dy} \frac{dy}{dx} = p \frac{dp}{dy}$$

$$yp \frac{dp}{dy} + p^2 = 0 \rightarrow y \frac{dp}{dy} + p = 0$$

$$\frac{dp}{p} = -\frac{dy}{y}$$


$$\ln p = -\ln y + c'$$

$$p = c' / y$$

$$p = \frac{dy}{dx} = \frac{c'}{y} \quad ydy = c'dx$$

$$\frac{1}{2}y^2 = c'x + c'' \quad y^2 = c_1x + c_2$$

# LRC Circuits

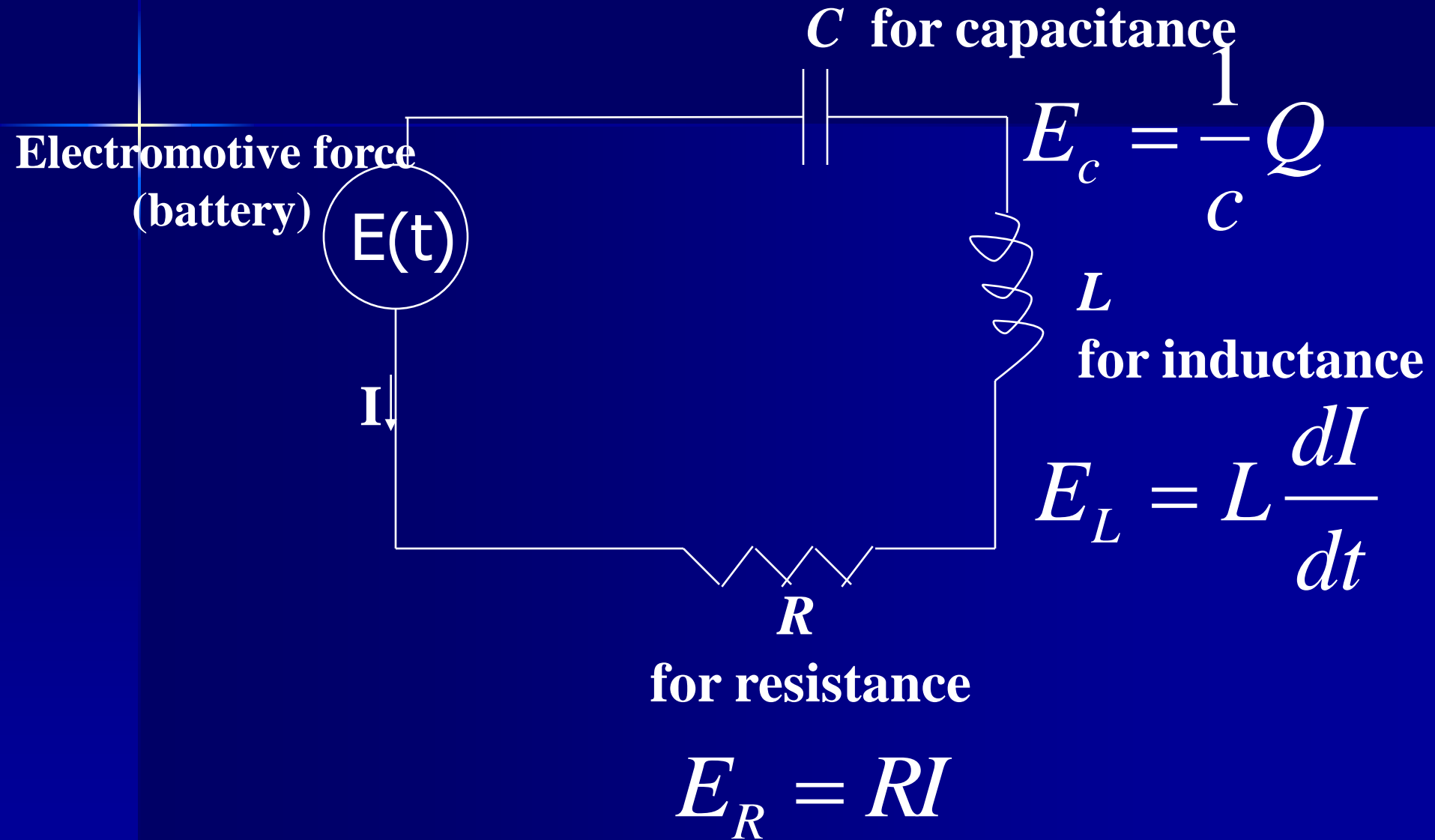

# Kirchoff's Law

**“The sum of the voltage drops across the passive elements in the circuit equals the applied voltage.”**

**Passive elements: inductor, resistor, capacitor**

**Applied voltage: what the battery supplies**

## The Model

$$E(t) = L \frac{dI}{dt} + RI + \frac{1}{C} Q$$

**Independent variable  $t$**

**Dependent variable  $I, Q$**

**Two dependent variables are o.k. for a partial d.e. or for a system.  
This model should only have one dependent variable.**

$$I = dQ / dt$$



$$E(t) = L \frac{dI}{dt} + RI + \frac{1}{C} Q$$



$$\frac{dI}{dt} = \frac{d^2Q}{dt^2}$$

$$I = \frac{dQ}{dt}$$



$$E(t) = L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q$$

# Example 1: RL-circuit

( Kirchhoff's voltage law )

$$E_L + E_R = E_0$$
$$L \frac{dI}{dt} + RI = E_0$$
$$\frac{dI}{E_0 - RI} = \frac{1}{L} dt$$

$$t = 0, \quad I = I_0$$

$$\ln(E_0 - RI) = -\frac{R}{L}t + \ln(E_0 - RI_0)$$

$$I = \frac{E_0}{R} + \left(I_0 - \frac{E_0}{R}\right)e^{-Rt/L}$$

*if*  $t \rightarrow \infty \Rightarrow E_0 = RI$

*if*  $I_0 = 0 \rightarrow I = \frac{E_0}{R} (1 - e^{-Rt/L})$

*if*  $E_0 = 0 \rightarrow I = I_0 e^{-Rt/L}$



*For Your Attention*